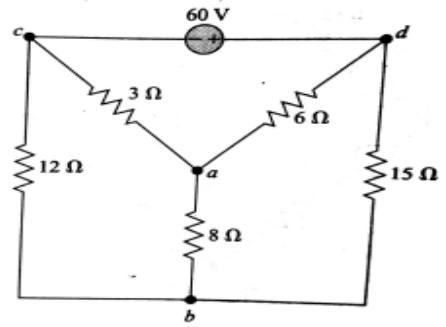
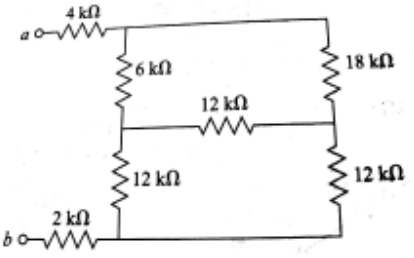


Time: 3 Hours

Max. Marks: 100

Note: (i) Answer Five full questions selecting any one full question from each Module.

(ii) Question on a topic of a Module may appear in either its 1st or/and 2nd question.

		Module-1	Marks
1	a.	Derive the expression for i) Δ to Y transformation ii) Y to Δ transformation.	10
	b.	Using source shifting and source transformation techniques, calculate V_{ad} for the circuit shown in Fig.Q1 (b).  Fig. Q1(b)	10
		OR	
2	a.	Determine the equivalent resistance across the terminals a and b, shown in Fig.Q2(a)  Fig.Q2(a)	5
	b.	Determine the value of v_x using mesh analysis for Fig.Q2 (a) shown below.	5

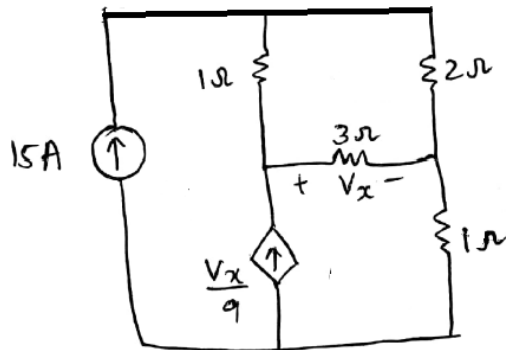


Fig.Q2(a)

- c. For the network of Fig.Q2(b), determine the node voltage by nodal analysis.

10

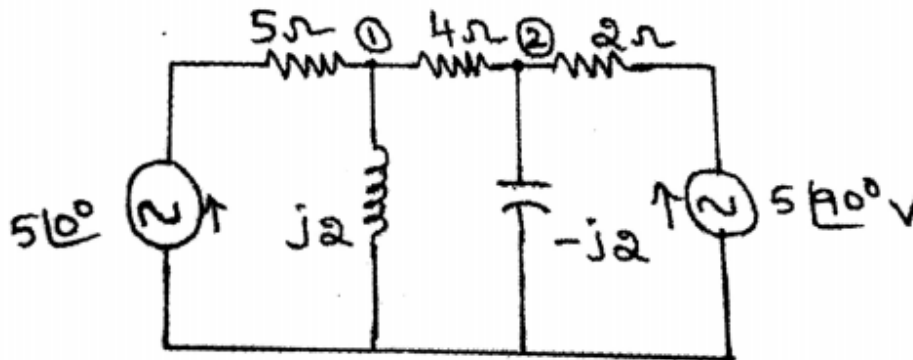


Fig.Q2(b)

Module-2

- 3 a. State superposition theorem. In the circuit of Fig.Q3(a), use the superposition principle to determine the value of i_x .

10

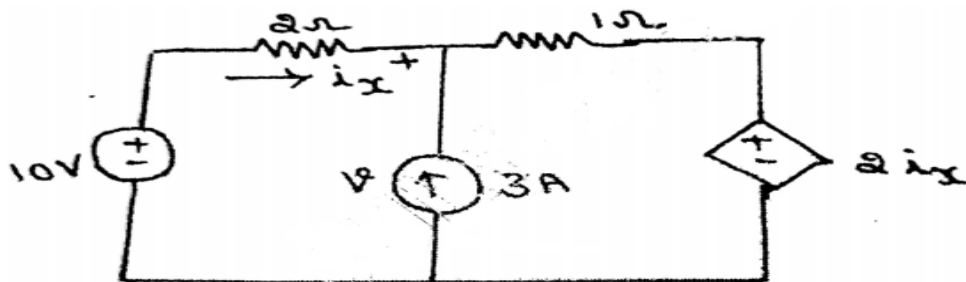


Fig.Q3(a)

- b. Obtain the Thevenin's and Norton's equivalent for the network shown in Fig.Q3 (b).

10

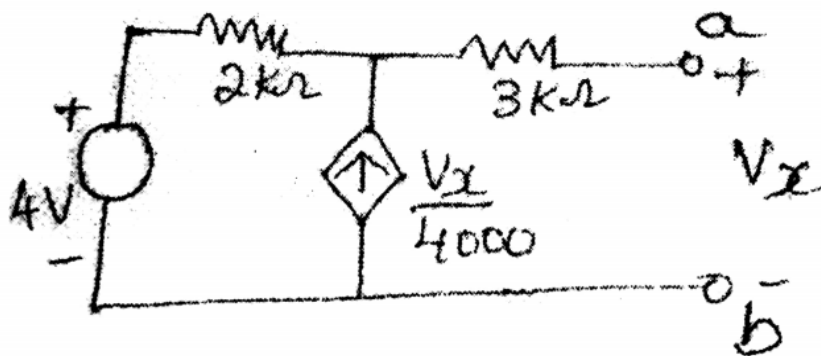


Fig.Q3(b)

OR

4 a. State and explain maximum power transfer theorem. 4

b. Using Millman's theorem, find I_L through R_L for the network shown in Fig.Q4 (b). 6

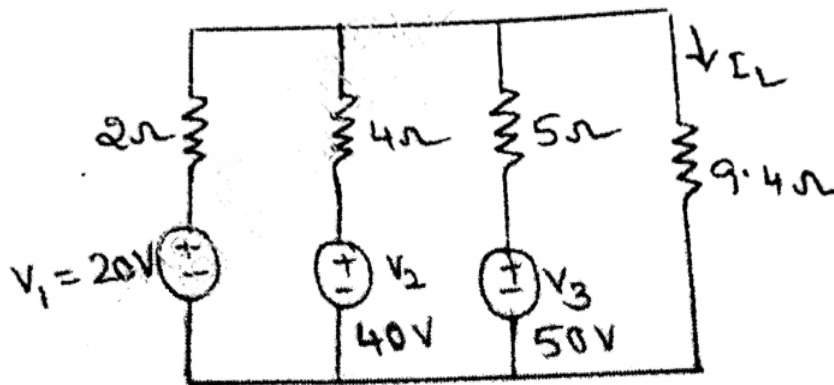


Fig.Q4(b)

c. State and verify reciprocity theorem for the circuit shown in Fig.Q4(c). 10

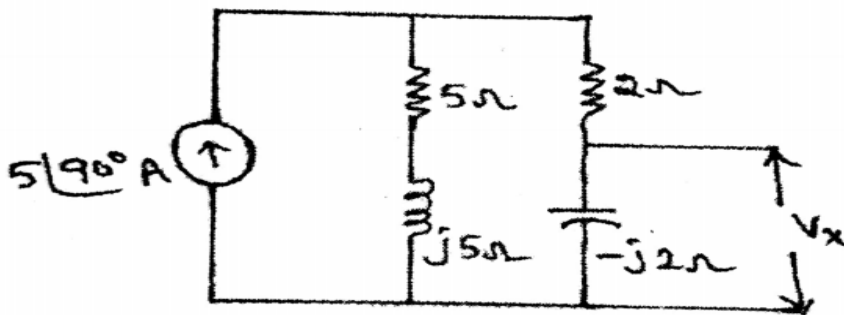





Fig.Q4(c)

Module-3

5 a. State and prove initial value theorem and final value theorem. 10

b. In the circuit shown in Fig.Q5(b), the switch was in position a for sufficiently long time to have achieved steady state. At $t=0$, the switch

		<p>was changed from a to b. Determine i_L and V_C, their first and second order derivatives at $t=0+$.</p> <p>Fig.Q5 (b)</p>	
		OR	
6	a.	<p>The switch in the network shown in Fig.Q6 (a) is closed at $t=0$. Determine the voltage across capacitor. Use Laplace transform.</p> <p>Fig.Q6(a)</p>	10
	b.	<p>Determine the Laplace transform of the periodic saw tooth waveform of Fig.Q6 (b). Use gate function.</p> <p>Fig.Q6 (b)</p>	10
		Module-4	
7	a.	<p>What is resonance? Derive an expression for half power cutoff frequencies.</p>	8
	b.	<p>Define Q-factor, resonant frequency, selectivity and bandwidth.</p>	4
	c.	<p>A series RLC circuit consists of $R=10\Omega$, $L=0.01H$ and $C=0.01\mu F$ is connected across a supply of $10mV$. Determine, i) f_0 ii) Q-factor iii) BW iv) f_1</p>	8

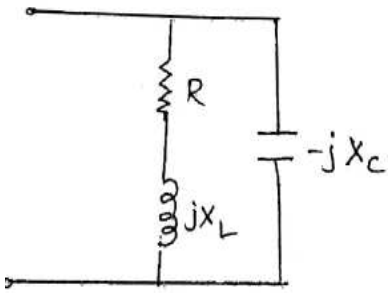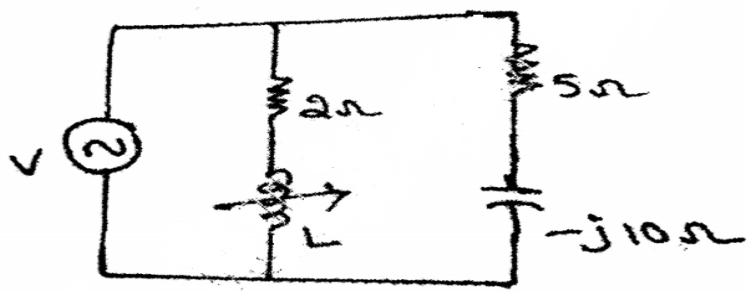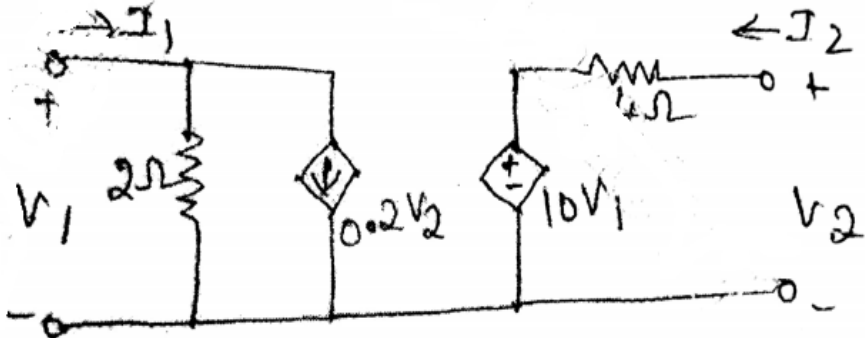		and $f_2 v)I_0$.	
		OR	
8	a.	Prove that for a series resonant circuit, the resonant frequency is the geometric mean of two half power frequencies.	4
	b.	Obtain the expression for the resonant frequency for the circuit shown in Fig.Q8 (b).	8
		 <p style="text-align: center;">Fig.Q8 (b)</p>	
	c.	Find the value of L for which the circuit shown in Fig.Q8(c) is resonant at a frequency of $\omega=5000$ rad/sec.	8
		 <p style="text-align: center;">Fig.Q8(c)</p>	
		Module-5	
9	a.	Define y-parameters. Also, find y-parameters for the two-port network shown in Fig.Q9 (a).	10
		 <p style="text-align: center;">Fig.Q9 (a).</p>	

	b.	Define ABCD parameters. Express y-parameters in terms of ABCD parameters.	10
		OR	
10	a.	Define hybrid parameters (h). Express hybrid parameters in terms of impedance parameters (z).	10
	b.	Define z parameters. Also, find z parameters for the network shown in Fig.Q10 (b).	10

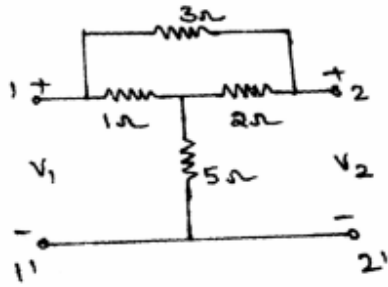


Fig.Q10 (b).
