

Third Semester B E Degree Examination, December 2018

Electric Circuit Analysis



Time: 3 Hours

Max. Marks: 100

Note: Answer FIVE full Questions choosing one full question from each module.

1.

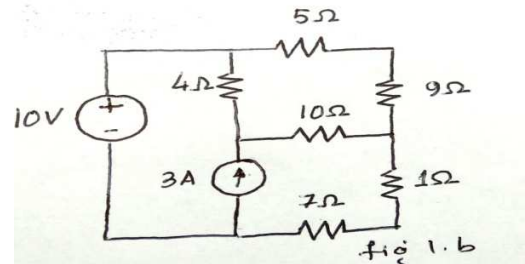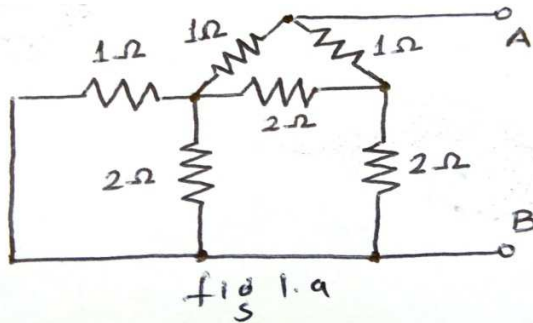- a. Reduce the network into equivalent circuit between A & B terminals by star-delta transformation for the network shown in fig (1.a). 10M





- b. Using mesh current analysis finds loop currents for the circuit shown in fig (1.b). 10M

OR

2.

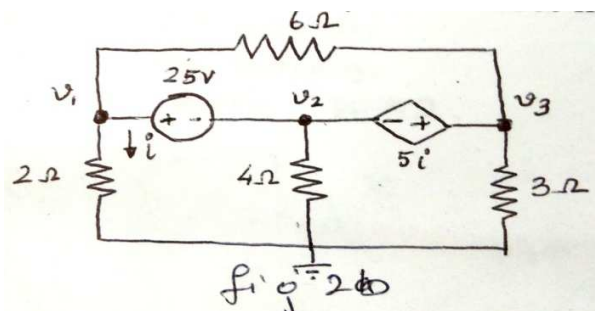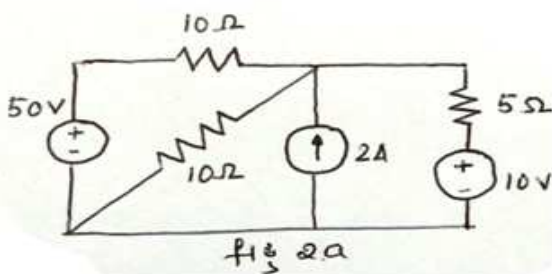- a. Using source transformation find the power delivered by 50 V source in given network of fig 2 (a) 10M




- b. Find all node voltages for the circuit shown in fig (2.b) using node analysis.

3.

a. State and prove Superposition Theorem. 10M

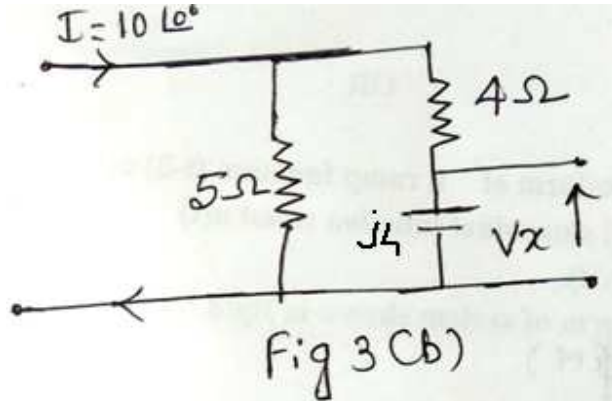b. Prove Reciprocity Theorem for the circuits shown in fig (3.b). 10M





OR

4.

a. Find the Thevenin's equivalent ckt of the ckt shown in fig(4.a). 10M

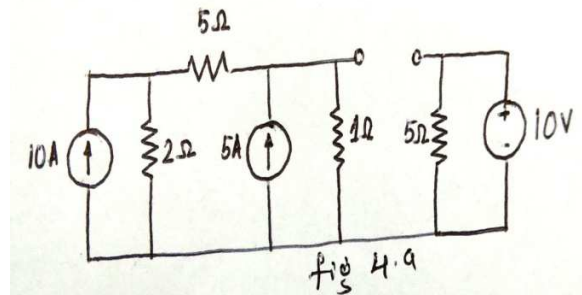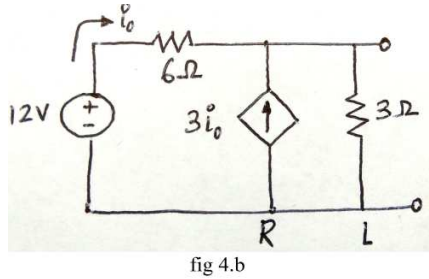b. Find Norton's equivalent circuit at the terminals shown in fig (4.b). 10M



5.

a. Show that in series resonant circuit the resonant frequency is equal to the geometric mean of half power frequencies. 10M

b. A two branch anti resonance ckt contains $L=0.4H$ & $C=40 \text{ microF}$. Resonance is to be achieved by variation of R_L & R_C . calculate the resonant frequency for the following cases 10M

i. $R_L=120 \text{ ohm}$, $R_C=80 \text{ ohm}$

ii $R_L=100 \text{ ohm}$, $R_C=100 \text{ ohm}$

OR


6.

a. Show that

i. The voltage of a capacitor cannot Change instantly. 10M


ii The current in an inductor cannot change instantly.

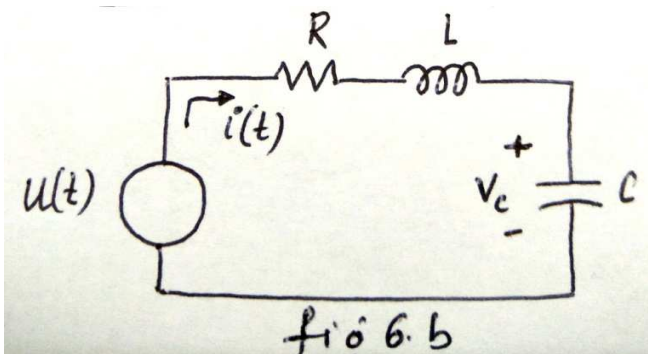- b. For the ckt shown in fig (6.b) find V_c at $t=0^+$ & $t=\infty$ 10M



7.

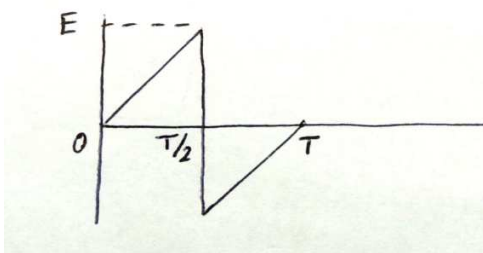
- a. State and Prove Initial and final value theorem. 10M
 b. Find Laplace of the saw tooth waveform shown in fig 7.b 10M



OR

8.

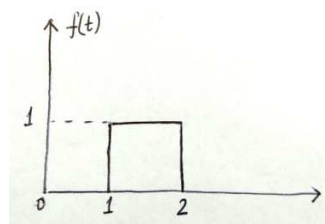- a. Obtain the Laplace transform of i) ramp function $(t-2)u(t)$ ii) exponential function $e^{-at}u(t)$ iii) sinusoidal function $\sin\omega t u(t)$ iv) $V(t)=4u(t-2)-3u(t)$ v) impulse function $\delta(t)u(t)$. 10M
 b. Obtain Laplace Transform of system shown in fig(8.b). 10M



9.

- a. Define two port networks and Give expression for T parameters. 10M
 b. Following short circuit currents and voltages are obtained experimentally for a two port network: Determine Y parameters 10M
- i) With output short circuited $I_1= 5\text{mA}$; $I_2=-0.3\text{mA}$ and $V_1=25\text{ V}$
 ii) With input short circuited $I_1= -5\text{mA}$; $I_2=10\text{mA}$ and $V_2=30\text{ V}$

OR

10.

- c. Express Z parameters in terms of Y parameters. 10M
- d. Following are the hybrid parameters for a network Determine the Y parameters for the network 10M

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 5 & 2 \\ 3 & 6 \end{bmatrix}$$