

Model Question Paper-1 with effect from 2019-20 (CBCS Scheme)

USN

--	--	--	--	--	--	--	--	--	--

Fourth Semester B.E. Degree Examination Subject Title: Analog Circuits

TIME: 03 Hours

Max. Marks: 100

Note: Answer any **FIVE** full questions, choosing at least **ONE** question from each **MODULE**.

Module -1			*Bloom's Taxonomy Level	Marks
Q.01	a	Explain the design constraints of a classical discrete-circuit biasing arrangement with circuit and relevant equations. How does R_E provide a negative feedback action to stabilize the bias current?	L2	8
	b	Considering the conceptual circuit of common emitter configuration, derive the expressions for g_m , r_{π} , and r_e . Draw the hybrid $-\Pi$ model of a transistor.	L1,L2	8
	c	A BJT having $\beta=120$ is biased at a DC collector current of 1 mA. Find the value of g_m , r_e , r_{π} at the bias point .	L3	4
OR				
Q.02	a	Design a fixed V_G bias circuit using Voltage divider arrangement to establish a DC drain current of 0.5mA. The MOSFET is specified to have $V_t=1V$, $K_n'W/L=1mA/V^2$ $\{\lambda = 0\}$. Use $V_{DD} = 12V$. Calculate the percentage change in the value of I_D obtained when the MOSFET is replaced with another MOSFET having the same $k_n'W/L$ but $V_t = 1.5V$.	L3	10
	b	Explain the MOSFET biasing technique using a large drain-to-gate feedback resistance R_G . Design the drain-to-gate feedback biasing circuit to operate at a DC drain current of 0.5mA. Assume $V_{DD} = 5V$, $k_n'W/L=1mA/V^2$, $\lambda=0$.	L3	6
	c	Draw and explain the small signal model of the MOSFET assuming $\lambda \neq 0$.	L1	4
Module-2				
Q.03	a	With a neat circuit diagram and ac equivalent circuit derive the expressions for R_{in} , A_{vo} , A_v and R_o for common source amplifier with an unbypassed source resistance.	L2	8
	b	Explain the internal capacitances of a MOSFET and hence draw the high frequency small signal model of MOSFET.	L1,L2	6
	c	For the n-channel MOSFET with $t_{ox}=10nm$, $L=1\mu m$, $W=10\mu m$, $L_{OV}=0.05\mu m$, $C_{sbo} = C_{dbo} = 10fF$, $V_O=0.6V$, $V_{SB}=1V$ and $V_{DS}=2V$. Calculate i) C_{OX} ii) C_{OV} iii) C_{gs} iv) C_{gd} v) C_{sb} vi) C_{db}	L3	6
OR				
Q.04	a	Derive the expression for low frequency response of a common source amplifier.	L1,L2	8
	b	It is desired to design a phase-shift oscillator (Self biased JEFT amplifier) using a JEFT having $g_m=5000\mu s$, $r_d = 40k\Omega$, and feedback circuit resistance of $R=10k\Omega$. Select the value of 'C' for oscillator operation at 1 kHz and R_D for a gain $A=40$ to ensure oscillator action.	L3	4

	c	With a neat diagram explain working of a crystal oscillator. Explain series and parallel resonance action with equivalent circuits and relevant expressions. A crystal has $L=0.334\text{H}$, $C=0.065\text{pF}$, $C_M=1\text{pF}$ and $R=5.5\text{k}\Omega$. Calculate its series and parallel resonant frequency.	L3	8
Module-3				
Q. 05	a	With a neat block diagram explain the working of a negative feedback amplifier. How is the overall gain affected in these amplifiers?	L1,L2	8
	b	Determine the voltage gain, input and output impedance with feedback for a voltage series feedback amplifier having $A= -100$, $R_i=10\text{k}\Omega$, $R_o=20\text{k}\Omega$ for a feedback of i) $\beta=1$ and ii) $\beta= -0.5$	L3	8
	c	Draw the four basic negative-feedback topologies.	L1	4
OR				
Q. 06	a	Define power amplifiers and list the types of power amplifiers based on the location of Q point, conduction angle, efficiency and applications.	L1,L2	8
	b	Prove that the maximum conversion efficiency of a transformer coupled Class A amplifier is 50%.	L2	6
	c	Calculate the efficiency of a transformer coupled Class B amplifier for a supply of 12V and peak output voltage of 6V.	L3	2
	d	Explain in brief the working of a Class C power amplifier.		4
Module-4				
Q. 07	a	How does negative feedback affect the performances of an inverting amplifier using opamp? Derive the relevant expressions for Gain, input resistance and output resistance.	L2	8
	b	The opamp 714C is connected as an inverting amplifier with $R_1=1\text{k}\Omega$ and $R_F=4.7\text{k}\Omega$. Compute the closed loop parameters: A_F , R_{IF} , R_{OF} , f_F . Given $A=400000$, $R_i=33\text{M}\Omega$ and $R_o=60\Omega$; supply voltages are $\pm 13\text{V}$; Max output voltage swing = $\pm 13\text{V}$, Unity gain bandwidth = 0.6MHz .	L3	6
	c	With a neat circuit diagram explain the opamp based inverting scaling amplifier and averaging circuit with relevant expressions for the output.	L1,L2	6
OR				
Q. 08	a	What is an instrumentation amplifier? What are its applications? With a neat circuit diagram explain an instrumentation amplifier using a transducer bridge.	L1,L2	10
	b	Draw the circuit and waveforms for an inverting Schmitt Trigger using opamp, with relevant expressions.	L1	4
	c	For an inverting Schmitt Trigger circuit $R_1 = 15\text{k}\Omega$; $R_2 = 1\text{k}\Omega$ and $V_{in} = 10\text{V}_{p-pp}$ sine wave. The saturation voltages are $\pm 14\text{V}$ and $V_{ref} = 2\text{V}$. i) Determine the threshold voltages V_{ut} and V_{lt} . ii) Find the value of Hysteresis voltage V_{hy} .	L3	6
Module-5				
Q. 09	a	Explain the working of a Successive Approximation type of ADC.	L2	8
	b	Explain with a neat circuit diagram, the working of a small signal half wave precision rectifier using an Opamp.	L2	4
	c	What is R-2R network type DAC? Explain with relevant expressions.	L1,L2	8
OR				
Q. 10	a	Explain the working of a second order high pass Butterworth filter with a neat circuit diagram and frequency response. Write the relevant design equations.	L1,L2	6
	b	Explain the operation of 555 timer as a Monostable multivibrator with relevant expressions.	L1,L2	8

	c	In an astable multivibrator $R_A = 2.2 \text{ K}\Omega$; $R_B = 3.9 \text{ K}\Omega$ and $C = 0.1 \mu\text{F}$. Determine the positive pulse width T_c and negative pulse width T_d and free running frequency ' f_o '.	L3	6
--	---	---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----	---

*Bloom's Taxonomy Level: Indicate as L1, L2, L3, L4, etc. It is also desirable to indicate the COs and POs to be attained by every bit of questions.