

# Model Question Paper- I

## CBCS SCHEME

### First/ Second Semester B.E Degree Examination,


### Fundamentals of Electronics and Communication Engineering(1BECE105/205)

TIME: 03 Hours

Max.Marks:100

Notes:

1. Answer any FIVE full questions, choosing at least ONE question from each MODULE
2. VTU Formula Hand Book is Permitted
3. M: Marks, L: Bloom's level, C: Course outcomes.

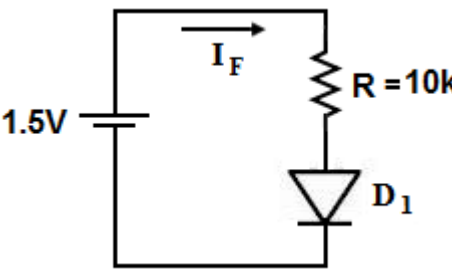Module - 1		M	L	C
Q.1	a What is a diode? Explain the operation of PN junction diode under forward and reverse bias condition.	8	L2	CO1
	b With circuit diagram explain the operation of full wave bridge rectifier. Draw the input and output waveforms.	8	L2	CO2
	c Calculate current in the circuit when a silicon diode connected in series with a resistor of 4.7 K $\Omega$ is driven by a 15V DC supply.	4	L3	CO1
OR				
Q.2	a Explain Zener as voltage regulator under no load and full load conditions.	8	L2	CO1
	b Explain the operation of half wave rectifier with capacitor filter.	8	L2	CO2
	c Calculate $I_F$ for the diode in the given circuit assuming that $V_F=0.7$ V and $r_d=0$ . What is the current if we consider $r_d=0.2\Omega$ .	4	L3	CO1
				
Module – 2				
Q.3	a Explain input and output characteristics of BJT in common emitter configuration.	8	L2	CO2
	b Explain various currents and voltages flowing through the BJT transistor.	8	L2	CO2
	c A transistor has $\beta=150$ and $I_E=12$ mA, Calculate the approximate collector current ( $I_C$ ) and Base current ( $I_B$ ).	4	L2	CO2
OR				
Q.4	a Explain the construction and characteristics of N-channel JFET.	8	L2	CO2
	b Explain N-channel enhancement type MOSFET and describe the construction and working.	8	L2	CO2
	c Define $\alpha$ and $\beta$ . Determine the relationship between $\alpha$ and $\beta$ .	4	L2	CO2

# Model Question Paper- I

Module – 3					
Q5	a	Explain block diagram of typical Op-Amp.	7	L2	CO2
	b	Explain the working of an Op-Amp as i) Subtractor ii) Voltage follower.	7	L2	CO2
	c	For a summing circuit if $V_1 = +1V$ , $V_2 = +3V$ and $V_3 = +2V$ with $R_f = 3K\Omega$ , $R_1 = R_2 = R_3 = 2K\Omega$ . Determine the output voltage.	6	L3	CO2
OR					
	a	Explain Op-Amp as an inverting and non-inverting amplifier.	7	L2	CO2
	b	Derive the expression for output voltage of an Op-Amp differentiator circuit.	7	L2	CO2
	c	Design an amplifier with a gain of +9 and $R_f = 12 K\Omega$ using an Op-Amp.	6	L3	CO2
Module – 4					
Q.7	a	With a block diagram explain the basic elements of a communication system.	7	L2	CO3
	b	Explain Amplitude modulation with neat waveforms,	7	L2	CO3
	c	Explain the concept of mobile wireless telephone systems,	6	L2	CO3
OR					
Q.8	a	Explain different communication channels and their characteristics.	7	L2	CO3
	b	With a block diagram, explain superheterodyne receiver,	7	L2	CO3
	c	Explain Phase modulation,	6	L2	CO3
Module – 5					
Q.9	a	State and prove DeMorgan's theorem for three input variables.	6	L3	CO5
	b	Subtract using 1's and 2's complement method. i) $(1001)_2$ from $(1101)_2$ ii) $(1101)_2$ from $(1001)_2$	7	L3	CO4
	c	Simplify the Boolean function to minimum number of literals i) $P = (xy + x'y + yz)$ ii) $P = (x'y + x(y+z) + y'z')$	7	L3	CO4
OR					
Q.10	a	Solve a) $(956.25)_{10} = (?)_2 = (?)_{16}$ b) $(111000111.010001)_2 = (?)_8 = (?)_{16}$	6	L3	CO5
	b	Express the Boolean function $F = XY + \overline{X}Z$ in product of maxterm form,	7	L3	CO4
	c	Construct and describe full adder with neat logic diagram and truth table. Implement using basic gates,	7	L3	CO4

# Model Question Paper- I

## CBCS SCHEME

### First/ Second Semester B.E Degree Examination,

#### Fundamentals of Electronics and Communication Engineering(1BECE105/205)

TIME: 03 Hours

Max.Marks:100

Notes:

1. Answer any FIVE full questions, choosing at least ONE question from each MODULE
2. VTU Formula Hand Book is Permitted
3. M: Marks, L: Bloom's level, C: Course outcomes.

Module - 1			M	L	C
Q.1	a	With appropriate circuit diagram, explain the DC load line analysis of a semiconductor diode.	7	L2	CO1
	b	With relevant diagrams explain ideal, practical and piecewise linear characteristic of a PN junction diode.	8	L2	CO1
	c	What is Filter? Explain the types of filters.	5	L2	CO1
OR					
Q.2	a	With the circuit diagram explain the operation of center tapped full wave rectifier. Draw the input and output waveforms.	8	L2	CO1
	b	Explain the operation of Zener diode along with its characteristics.	7	L2	CO1
	c	Calculate the forward and reverse resistances offered by a silicon diode with $I_F = 100\text{mA}$ , $V_F = 0.75\text{V}$ and $V_R = 50\text{V}$ , $I_R = 1\mu\text{A}$ .	5	L2	CO1
Module - 2					
Q.3	a	Explain input and output characteristics of the common Base configuration.	8	L2	CO2
	b	Explain depletion type MOSFET and describe the construction and working.	7	L2	CO2
	c	Calculate $\alpha_{dc}$ and $\beta_{dc}$ for the transistor if $I_C = 1\text{mA}$ and $I_B = 25\mu\text{A}$ . Determine the new base current to give $I_C = 5\text{mA}$ .	5	L3	CO2
OR					
Q.4	a	With neat circuit diagram, explain DC line concept of a transistor amplifier to fix the Q point.	8	L2	CO2
	b	Explain the construction and characteristics of P-channel JFET.	7	L2	CO2
	c	Calculate $I_C$ and $I_E$ for a transistor that has $\alpha_{dc} = 0.98$ and $I_B = 100\mu\text{A}$ . determine the value of $\beta_{dc}$ for the transistor.	5	L3	CO2

Module - 3					
Q5	a	Briefly discuss the ideal characteristics of the Op-Amp.	7	L2	CO2
	b	Derive the expression of voltage Gain of a i) Non inverting Op-Amp. ii) Inverting Op-Amp.	6	L2	CO2
	c	For an op-amp given the figure find the output voltage $v_{o1}$ and $v_{o2}$	7	L3	CO2

# Model Question Paper- I

OR					
Q.6	a	Derive the expression for output voltage of an Op-Amp Integrator circuit.	7	L2	CO2
	b	Define Op Amp Parameters. Gain, CMRR, Slew rate, input resistance.	6	L2	CO2
	c	Find an output voltage expression for the given circuit.	7	L3	CO2
Module – 4					
Q.7	a	Explain frequency modulation with neat waveforms.	10	L2	CO3
	b	Explain wireline, fiber optic and wireless electromagnetic communication channels.	10	L2	CO3
OR					
Q.8	a	Describe the process of AM radio broadcasting with a neat block diagram.	10	L2	CO3
	b	What is modulation? Need for modulation and different modulation schemes.	10	L2	CO3
Module – 5					
Q.9	a	Explain SOP & POS with examples.	6	L2	CO4
	b	Simplify the following Boolean functions: i) $(A + \overline{B}C)(\overline{A} + B + \overline{C})(A + \overline{B})$ ii) $A + A\overline{B} + \overline{A}B$	6	L3	CO5
	c	Solve a) $(A156.25)_{16} = (?)_2 = (?)_8$ b) $(10011.110101)_8 = (?)_2 = (?)_{10}$	8	L3	CO5
OR					
Q.10	a	Explain NAND and NOR gate called as universal gates.	6	L2	CO4
	b	Implement the following expression using logic gates $Y = A + C\overline{B} + \overline{A}BC$ $F = \overline{xy} + \overline{xz}$	6	L3	CO5
	c	Explain how a full adder can be reconfigured using two half adders. Draw the circuit.	8	L3	CO5