

Model Question Paper (CBCS Scheme)



USN									
-----	--	--	--	--	--	--	--	--	--


**Third Semester BE Degree Examination
Course Title–Electric Circuit Analysis**

TIME:03Hours


Max.Marks:100


Note: Answer any **FIVE** full questions, choosing at least **ONE** question from each **MODULE**.

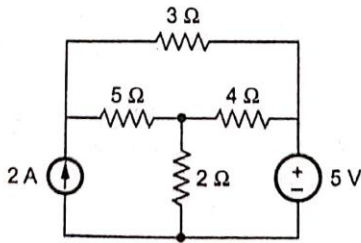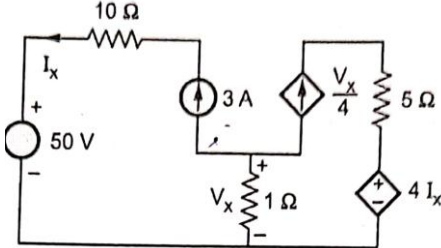
Q.No.	Module1	Marks
Q1	a Define the following networks with example a) Lumped and Distributed Network b) Bilateral and Unilateral Network c) Active and Passive network	06
	b Using source transformation and source shifting techniques, find voltage across 2-ohm resistor. 	07
	c Determine I_x and V_x for the circuit shown below using mesh analysis. 	07
OR		
a	Obtain expressions to convert Delta connected impedances into equivalent star connected impedances.	06
b	Explain the concept of super node using network and also mention steps to apply nodal analysis.	07

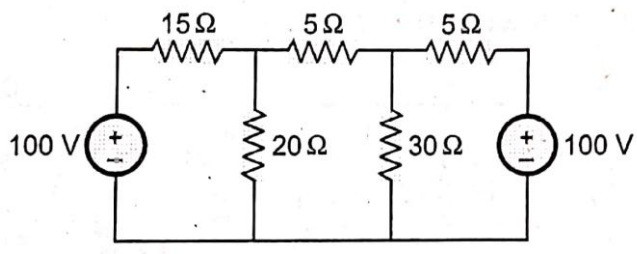Q2	c	<p>For the circuit shown below, find the current through 30ohm resistor using mesh analysis</p> 	07
----	---	--	----

Module 2


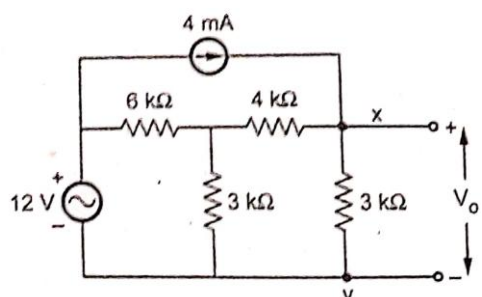
	a	<p>Obtain Thevenin's equivalent network shown in fig below, between terminals x and y also find V_0.</p> 	06
--	---	--	----

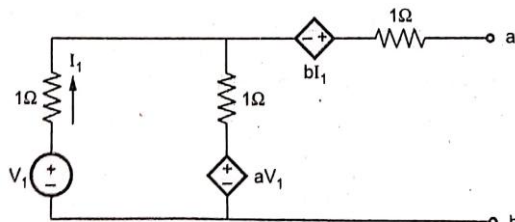Q3	b	<p>For the network shown below determine that Norton's equivalent at terminals a-b.</p> 	07
----	---	--	----

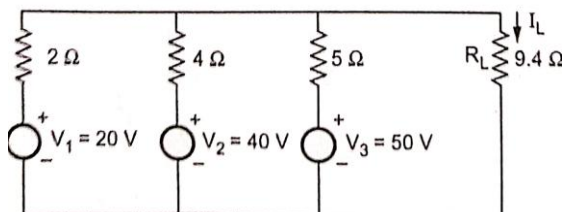
	c	<p>Using Milliman's theorem, find I_L through R_L for network shown below</p> 	07
--	---	--	----

OR

	a	<p>State and explain maximum power transfer theorem using suitable networks and also prove the maximum power transfer theorem.</p>	06
--	---	--	----

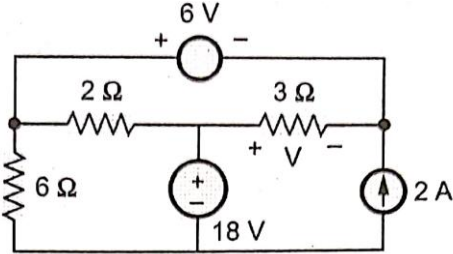
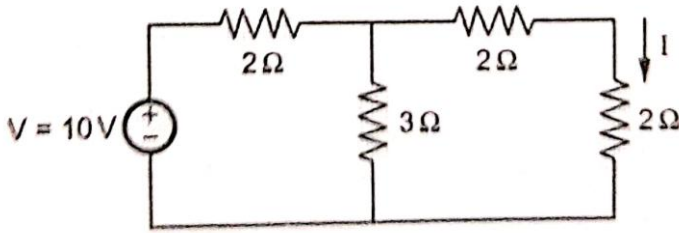
Q4	b	Find the voltage V across 3Ω resistor using superposition theorem for given circuit	07
			
Q4	c	Verify reciprocity theorem for voltage V and current I in network shown below	07
			

Module 3

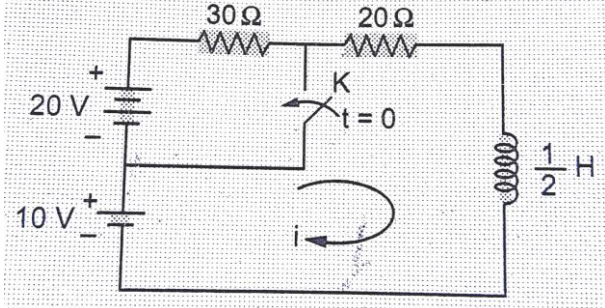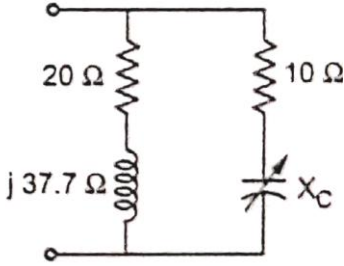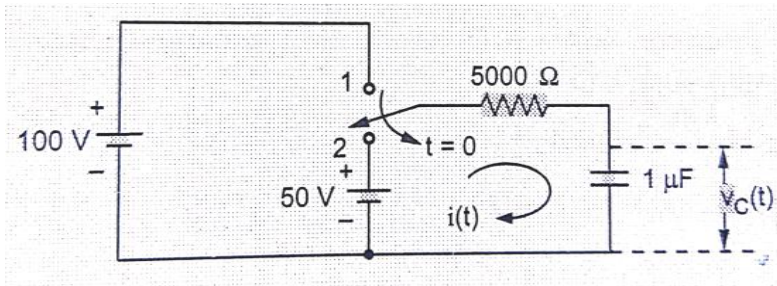
Q5	a	Define the following i) Resonance ii) Q-factor iii) selectivity iv) Bandwidth	06
	b	Explain the behavior of R, L, C elements for transients. Mention their representation at the time of switching.	07
	c	The network shown in fig below is under steady state condition with switch K is closed. Determine expression for $i(t)$ if switch K is opened.	07
			

OR


a	Show that at half power frequencies f_1 and f_2 , the reactive part of impedance of series RLC circuit is equal to resistive part of impedance.	06
---	---	----

Q6	b	For circuit shown in figure below determine two values of capacitor for resonance at $f=50\text{Hz}$.	07
			
	c	A switch is moved from position 1 to 2 at $t=0$. Find $V_R(t)$ and $V_C(t)$ for $t>0$.	07
			

Module 4

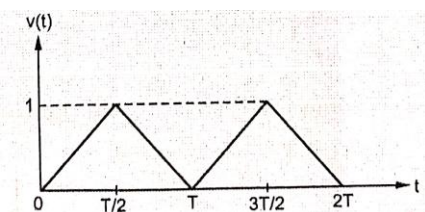Q7	a	Mention advantages and disadvantages of Laplace transform.	06
	b	State and Prove Final value theorem as applied to Laplace transform.	07
	c	Synthesis the waveform shown in fig below and Determine Laplace transform of periodic waveform.	07
			

OR

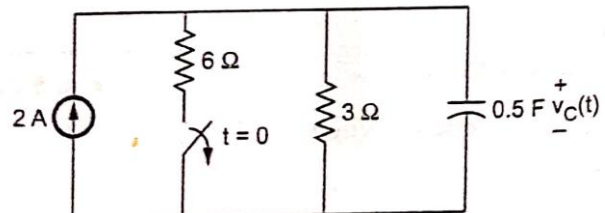Q8	a	Obtain Laplace transform of a Unit step function	06
	b	Determine Laplace transform of a following i) $\sin^2 t$ ii) $\cos^2 t$	07
	c	Calculate the voltage $V_C(t)$ for $t \geq 0$ for the circuit shown below using laplace transform method. In the circuit, switch is opened at $t=0$.	07
			

Module 5

Q9	a	Define port of network and write assumptions to be made to find network and also obtain y-parameter.	10
	b	An unbalanced 3 phase load is supplied by symmetrical 3 phase, 440V, 3 wire system. The star connected load branch are $Z_R=5\ 30$, $Z_Y=10\ 45$, $Z_B=10\ 60$. Determine line currents.	10
OR			
Q10	a	Discuss the method of analyzing 3-phase star connected unbalanced load using Milliman's Theorem and mesh method.	10
	b	Determine z-parameter of network shown below & give its equivalent circuit.	10

