

CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

18EC42

Fourth Semester B.E. Degree Examination, July/August 2021 Analog Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions.

- 1 a. Explain the voltage divider biasing for BJTs using single power supply. How does R_E provides a negative feedback action to stabilize the bias current with necessary supporting mathematical equations. (08 Marks)
- b. For the circuit shown in Fig.Q1(b), derive the expression of voltage gain.

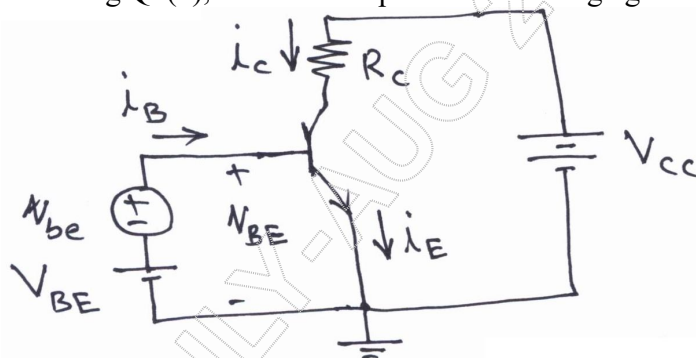


Fig.Q1(b)

(06 Marks)

- c. A BJT having $\beta = 100$ is biased at a dc collector current of 1 mA. Find the value of g_m , r_e and r_π at the bias point. Assume $V_T = \frac{1}{40}$ V (06 Marks)

- 2 a. For the circuit shown in Fig.Q2(a), find the required value of V_{GS} to establish a dc bias current $I_D = 0.5$ mA. Device parameters are $V_t = 1$ V, $K'_n \frac{W}{L} = 1$ mA/V² and $\lambda = 0$. What is the percentage change in I_D obtained when the transistor is replaced with another having $V_t = 1.5$ V.

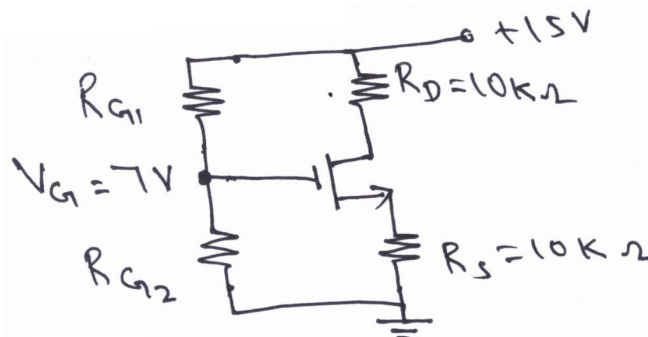


Fig.Q2(a)

(08 Marks)

- b. What is trans-conductance of a MOSFET and mention the three different expression used to calculate the trans-conductance. (06 Marks)
- c. Explain biasing of MOSFET by fixing V_{GS} . (06 Marks)

- 3 a. For the circuit shown in Fig.Q3(a), derive the expression of R_{in} , R_o , A_{V_o} and A_V using T-model.

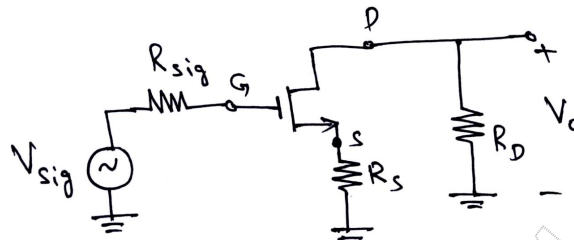


Fig.Q3(a)

(10 Marks)

- b. With mathematical equations, explain the different internal capacitances in the MOSFET. (10 Marks)

- 4 a. Explain the high frequency response of a CS amplifier using MOSFET and derive its upper cutoff frequency. (10 Marks)
- b. Explain the working principles of Colpitts oscillator and also discuss the drawback of this oscillator are over come using Clapp oscillator. (10 Marks)
- 5 a. In a particular circuit represented by the block diagram shown in Fig.Q5(a), a signal of 1V from the source results in a difference signal of 10 mV being provided to the amplifier (A) and 10V applied to the load. For this arrangement identify the value of A and β that apply.

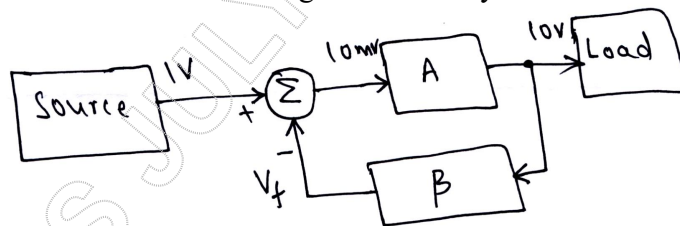


Fig.Q5(a)

(06 Marks)

- b. Draw the general feedback structure and explain with necessary expressions. (06 Marks)
- c. What are the properties of negative feedback and explain it. (08 Marks)

- 6 a. What is output stage and discuss the classification of output stages based on the collector current? (06 Marks)
- b. A transformer coupled class A power amplifier drawn a current of 200 mA from the collector supply of 10 V, when no signal is applied it. Determine:
- Maximum output power
 - Maximum collector efficiency
 - Power rating of the transistor
- If the load connected across the transformer secondary is $2\ \Omega$ and transformer turn ratio is 5:1. (06 Marks)
- c. Explain the working of class A output stage amplifier and also prove that power conversion efficiency is 25%. (08 Marks)

- 7 a. Derive the expression of exact voltage gain and ideal voltage gain of a voltage shunt feedback amplifier using OP-AMP. (08 Marks)
- b. The 741 OP-AMP having the following parameter is connected as a non-inverting amplifier with $R_1 = 1\text{ K}\Omega$ and $R_F = 10\text{ K}\Omega$. Given $A = 200000$, $R_i = 2\text{ M}\Omega$, $R_o = 75\ \Omega$, $f_0 = 5\text{ Hz}$ and supply voltage = $\pm 15\text{ V}$. Compute the value of A_F , R_{iF} , R_{oF} and f_F . (06 Marks)
- c. With the circuit and waveforms, explain the working of non-inverting comparator. (06 Marks)

- 8 a. Explain the working of instrumentation amplifier using transducer bridge and derive the expression of output voltage. (10 Marks)
- b. Explain the operation of a inverting Schmitt Trigger. (06 Marks)
- c. The circuit shown in Fig.Q8(c) is to be used as averaging amplifier with the following specifications: $V_a = V_b = 1.5\text{ V}$, $V_c = 3\text{ V}$, $R_1 = R = 1.5\text{ K}$ and $V_0 = 5.2\text{ V}$. Determine the required value of R_F .

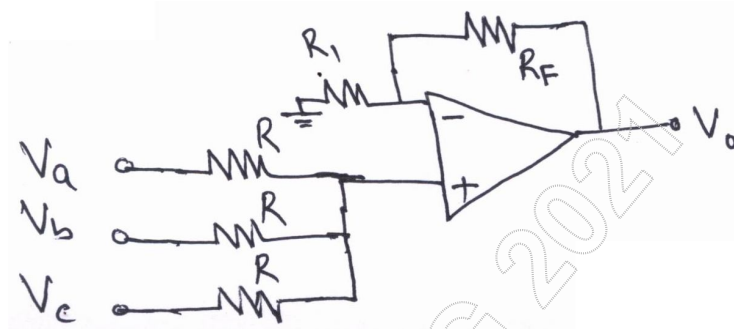


Fig.Q8(c)

(04 Marks)

- 9 a. Derive the expression of output voltage of a binary weighted resistor type DAC. (08 Marks)
- b. For the DAC using an R-2R network with $R = 10\text{ K}\Omega$, $R_F = 27\text{ K}\Omega$ and $V_R = 5\text{ V}$.
 (i) Determine the size of each step
 (ii) Calculate the output voltage when $b_0 = b_1 = b_2 = b_3 = 5\text{ V}$. (06 Marks)
- c. Explain the working of a first order active low pass filter with circuit and frequency response. (06 Marks)
- 10 a. Explain the operation of a successive approximation DAC and mention its advantages. (08 Marks)
- b. Mention the applications of 555 IC Timer. (04 Marks)
- c. Design an Astable Multivibrator using 555 IC Timer with
 (i) $f_0 = 1\text{ kHz}$ and $D = 40\%$
 (ii) $f_0 = 2\text{ kHz}$ and $D = 50\%$
 (iii) $f_0 = 1\text{ kHz}$ and $D = 70\%$
 Assume $c = 0.01\text{ }\mu\text{F}$ for all cases. (08 Marks)
