

--	--	--	--	--	--	--	--	--	--

Seventh Semester B.E. Degree Examination, July/August 2022

Digital System Design using VHDL

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain the four ways of simplifying a logic expression using the laws and theorems of Boolean Algebra. (10 Marks)
- b. Derive a Mealy state graph and state table for BCD to Excess-3 code converter. (10 Marks)

OR

- 2 a. Explain the 4 different coding schemes used for serial data transmission in Moore sequential network. Represent the following bit sequence transmission in all the code schemes: 01110010. (10 Marks)
- b. Using state equivalence theorem and state reduction technique solve for the final reduced table of the given state table. (10 Marks)

Present state	Next state		Present output	
	X = 0	X = 1	X = 0	X = 1
a	c	f	0	0
b	d	e	0	0
c	h	g	0	0
d	b	g	0	0
e	e	b	0	1
f	f	a	0	1
g	c	g	0	1
h	c	f	0	0

Module-2

- 3 a. Using VHDL process, write the VHDL program to model a JK flipflop that has active low direct set (SN) and direct reset (RN) inputs to change the state in the falling edge of the clock. (10 Marks)
- b. List and explain the predefined VHDL operators. (10 Marks)

OR

- 4 a. Write the VHDL program using single VHDL process with wait statement to model the behavior of BCD to Excess-3 mealy sequential network. (10 Marks)
- b. With the syntax, explain the entity-architecture pairs used to write the VHDL program. Write the VHDL program for full adder. (10 Marks)

Module-3

- 5 a. List and explain the scalar type VHDL data types. (10 Marks)
- b. List and explain the different styles of descriptions used to write a VHDL program. (10 Marks)

OR

- 6 a. With a neat logic symbol, logic diagram and truth table, write the data flow description of half adder. (08 Marks)
- b. Design a 2×2 unsigned combinational array multiplier and write the data flow description for the same. (12 Marks)

Module-4

- 7 a. With a neat diagram, explain the basic ROM structure. (06 Marks)
- b. Realize AND-OR array [PLA] for the given functions and also write the PLA table for the same.

$$\begin{array}{l} \text{Functions} \rightarrow F_0 = A'B' + AC' \\ F_1 = B + AC' \end{array} \quad \left| \quad \begin{array}{l} F_2 = A'B' + BC' \\ F_3 = AC + B \end{array} \right.$$

- c. With a neat diagram, explain combinational PAL segment. (07 Marks)

OR

- 8 a. With a neat block diagram, state graph and state table, explain the design of serial adder with accumulator. (10 Marks)
- b. With a neat block diagram and state graph, explain the design of a binary multiplier. (10 Marks)

Module-5

- 9 a. For the given logic symbol, write the truth table, logic diagram and VHDL code for the signal assignment statement $y = 2 * x + 3$. (10 Marks)

 


Fig.Q.9(a)

- b. With the example, explain the following VHDL statements:
i) If Statement ii) For Loop Statement. (10 Marks)

OR

- 10 a. With a neat diagram, explain the following:
i) Testing AND and OR gates for stuck-at faults
ii) Testing AND-OR network (2 level). (10 Marks)
- b. With a neat diagram, explain the standard Mealy sequential network and the corresponding iterative network. (10 Marks)

* * * * *