

USN

--	--	--	--	--	--	--	--	--	--

18EI/BM34

Third Semester B.E. Degree Examination, July/August 2022

Digital Design and HDL

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Define Minterm and Maxterm Canonical form. Give an example for each. (04 Marks)
- b. Simplify $f(A, B, C, D) = \sum m(2, 3, 4, 5, 13, 15) + \sum d(8, 9, 10, 11)$ using K – map. Implement the circuit using logic gates. (08 Marks)
- c. Using QM technique reduce the following Boolean equation
 $f(a, b, c, d) = \sum m(0, 1, 2, 3, 8, 9)$. (08 Marks)

OR

- 2 a. Define sum of product and product of sum. Give an example for each. (04 Marks)
- b. Convert $f_1 = a\bar{b} + a\bar{c} + bc$ into minterms and canonical form. $f_2 = (a + \bar{b})(\bar{b} + c)$ into maxterms, Canonical forms. (06 Marks)
- c. Simplify the equation using QM technique.
 $D = f(a, b, c, d) = \sum(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$. (10 Marks)

Module-2

- 3 a. Design a full subtractor using logic gates. (08 Marks)
- b. Implement the following using 74138(3 to 8) decoder. $f_1(a, b, c) = \sum m(0, 4, 6, 7)$,
 $f_2(a, b, c) = \pi m(2, 3, 6, 7)$. (06 Marks)
- c. Realize 4 : 1 MUX using basic gates. (06 Marks)

OR

- 4 a. What are the disadvantages of ripple carry adder? Explain how it can be overcome by carry look ahead adder. (08 Marks)
- b. Construct a 4 to 16 line decoder using two 74138 IC. (06 Marks)
- c. Design a combinational logic circuit using PROM for the following Boolean expression.
 $f_1(x_2, x_1, x_0) = \sum m(0, 1, 2, 5, 7)$; $f_2(x_2, x_1, x_0) = \sum m(1, 2, 4, 6)$. (06 Marks)

Module-3

- 5 a. With neat logic diagram and truth table, explain the working of SR latch. (08 Marks)
- b. Explain the working of Master slave JK flip flop with functional table and timing diagram. (08 Marks)
- c. Derive the characteristic equation of D flip flop. (04 Marks)

OR

- 6 a. With neat diagram, explain the working of positive edge triggered D flip flop. (10 Marks)
- b. With neat circuit and timing diagram, explain the application of SR flip flop as a switch debouncer. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

Module-4

- 7 a. Explain the working of Universal shift register along with its mode control table. (10 Marks)
 b. With neat logic diagram and timing diagram, explain 4 bit ripple up counter using T flip flop. (10 Marks)

OR

- 8 a. Design a mod 6 counter using JK flip flop to generate the following sequence.
 $0 \rightarrow 2 \rightarrow 3 \rightarrow 6 \rightarrow 5 \rightarrow 1 \rightarrow 0$. (10 Marks)
 b. Design Shift register based ring counter and Johnson counter. (10 Marks)

Module-5

- 9 a. Explain the following verilog operators :
 i) Reduction logic operators ii) Relational operators iii) Arithmetic operators
 iv) Shift operators v) Boolean logic operators. (10 Marks)
 b. Explain the following data types in verilog with example :
 i) Parameter ii) Arrays. (04 Marks)
 c. Write the verilog description of full adder using dataflow description. (06 Marks)

OR

- 10 a. Illustrate if and else if sequential statements. (06 Marks)
 b. Illustrate the any 2 types of loop statements of verilog. (06 Marks)
 c. Write verilog behavioral description of 4:1 MUX along with its functional table and logic diagram. And also write its simulation waveform. (08 Marks)

* * * * *