

CBCS SCHEME

USN

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

18RA35

Third Semester B.Tech. Degree Examination, Feb./Mar. 2022 Analog and Digital Electronic Circuits

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

Module-1

- 1 a. Explain positive clipper circuit with input output waveform. (10 Marks)
- b. Design the bandpass filter shown in Fig Q1(b) so that $f_c = 1\text{KHz}$. $Q = 3$, $AF = 10$. Design the centre frequency to 1.5KHz, keeping AF and the bandwidth constant.

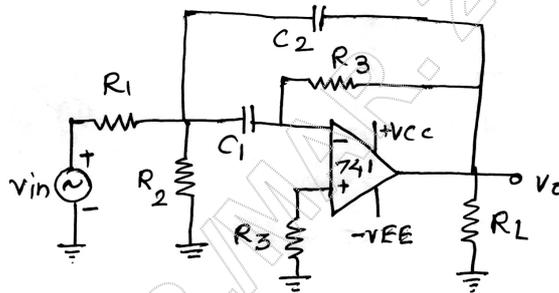


Fig Q1(b)

(10 Marks)

OR

- 2 a. With neat circuit diagram explain all pass filter. (10 Marks)
- b. Explain First order low pass Butterworth filter with frequency response. (10 Marks)

Module-2

- 3 a. Explain working of non inverting comparator with input and output waveform. (10 Marks)
- b. Explain with neat circuit diagram working, input, output waveform of phase shift oscillator. (10 Marks)

OR

- 4 a. In the circuit of inverting Schmitt trigger Fig Q4(a) $R_1 = 100\Omega$, $R_2 = 56\text{K}\Omega$, $V_m = 1\text{V}_A$ sine wave, and the opamp is type 741 with supply voltage = $\pm 15\text{V}$. Determine the threshold voltage V_{at} and V_{it} and draw the output waveform.

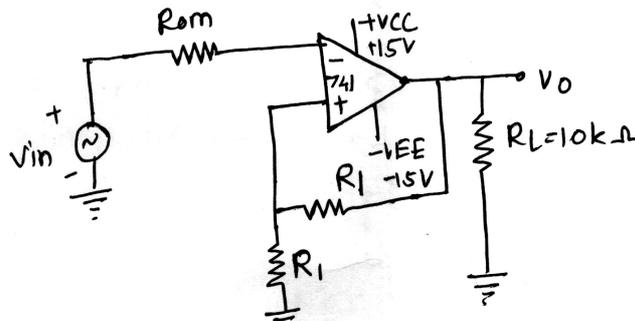


Fig Q4(a)

(10 Marks)

- b. Explain Wien Bridge oscillator with neat circuit diagram. Give expression for frequency of oscillation. (10 Marks)

Module-3

- 5 a. With neat waveform and circuit diagram, explain working of monostable multivibrator using 555 Timer. (06 Marks)
- b. In astable multivibrator of Fig Q5(b) $R_A = 2.2K\Omega$, $R_B = 3.9K\Omega$, $C = 0.1\mu F$. Determine the positive pulse width t_c , negative pulse width t_d and free running frequency f_o .

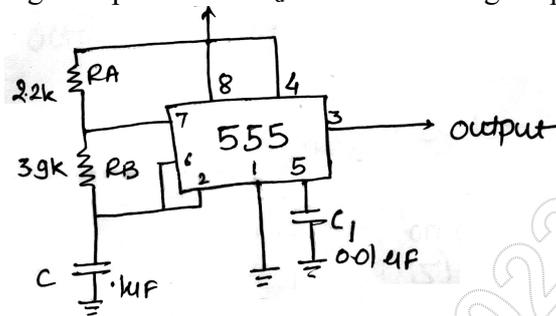


Fig Q5(b)

- c. Explain application of ICC555 astable multivibrator as square wave oscillator. (08 Marks)

OR

- 6 a. Show how IC555 timer can be used as an astable multivibrator. (10 Marks)
- b. In the circuit diagram Fig Q6(b) $R_A = 10K\Omega$, the output pulse width $t_p = 10ms$. Determine the value of C.

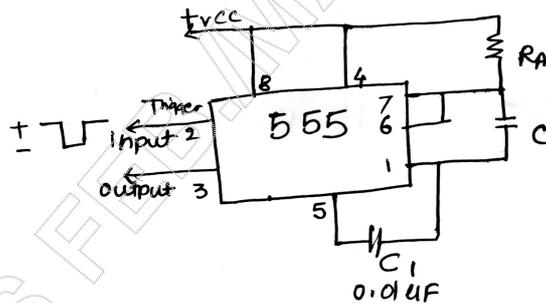


Fig Q6(b)

- c. Compare monostable multivibrators and astable multivibrators. (05 Marks)

Module-4

- 7 a. Simplify the Boolean function $f(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$. (06 Marks)
- b. Implement a full adder circuit with decoder and two OR gates. (06 Marks)
- c. Explain octal to binary encoder with logic diagram. (08 Marks)

OR

- 8 a. Simplify the following equation Kmap $F(A, B, C, D) = \Sigma(2, 4, 5, 13, 14) + \Sigma d(0, 1, 8, 10)$. (06 Marks)
- b. Implement the following function with multiplexer $f(A, B, C, D) = \Sigma(0, 1, 3, 4, 8, 9, 15)$ (06 Marks)
- c. Design BCD to decimal decoder. (08 Marks)

Module-5

- 9 a. With the help of timing diagram explain SR master slave Flip flop. (08 Marks)
- b. With neat circuit diagram, explain Binary ripple counter. (06 Marks)
- c. Explain T Flip flop with characteristics equation. (06 Marks)

OR

- 10 a. Explain the working of binary Up-Down counter. (08 Marks)
- b. Explain with neat diagram working of JK flip flop and derive its characteristic equation. (08 Marks)
- c. Differentiate between synchronous and asynchronous counter. (04 Marks)