

Model Question Paper-I with effect from 2023-24 (CBCS Scheme)

USN



--	--	--	--	--	--	--	--	--	--



Third Semester B.E. Degree Examination
Electronic Principles and circuits

TIME: 03 Hours

Max. Marks: 100

Note: 01. Answer any FIVE full questions, choosing at least ONE question from each MODULE.

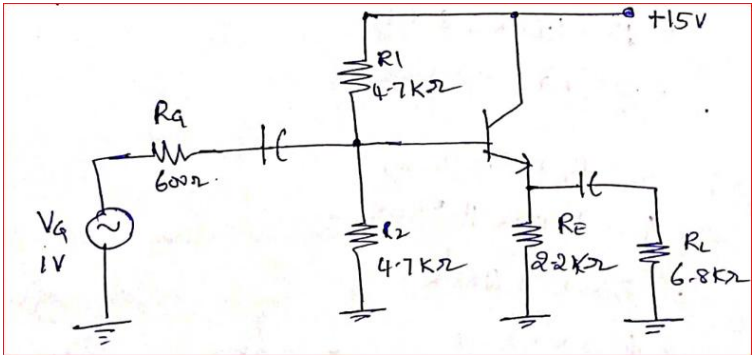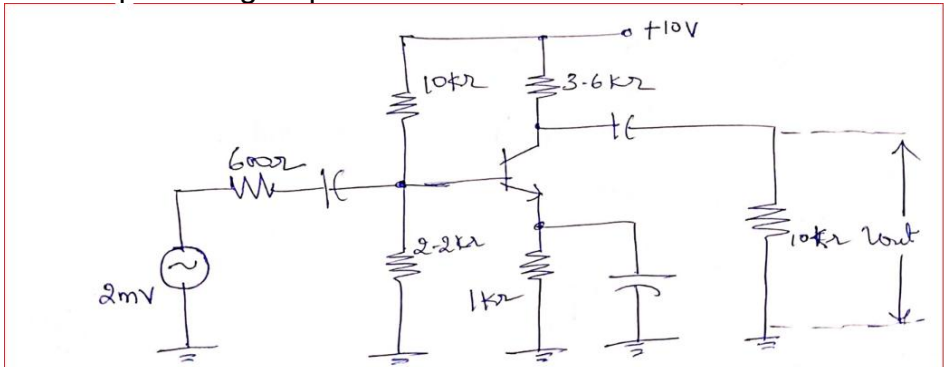Q.No	Question	Marks	Bloom's Level
MODULE-1			
1	a. Develop an expression for the operating point I_C and V_{CE} for the voltage divider bias circuit using approximate analysis. Also Calculate the operation point for the VDB circuit given $V_{CC}=10V$, $R_1=10K\Omega$, $R_2=2.2K\Omega$, $R_c=3.6K\Omega$, $R_E=1K\Omega$	10	L3
	b. For the circuit shown in Fig 1b, determine the voltage gain and ac load voltage if $\beta = 150$	10	L3
 <p style="text-align: center;">Fig 1b</p>			
OR			
2	a. Design the voltage divider bias circuit to meet the following specifications $V_{CC}=10V$, V_{CE} at mid point, stiff voltage divider, collector current 1mA, $\beta_{dc} = 70 -200$	10	L3
	b. For the circuit shown below in Fig 2b, the ac generator has an internal resistance of 600Ω for a voltage divider circuit. Determine the output voltage if $\beta = 300$	10	L3
 <p style="text-align: center;">Fig 2b</p>			
MODULE-2			
3	a. With neat circuit diagrams, explain biasing of MOSFET by fixing the	10	L3

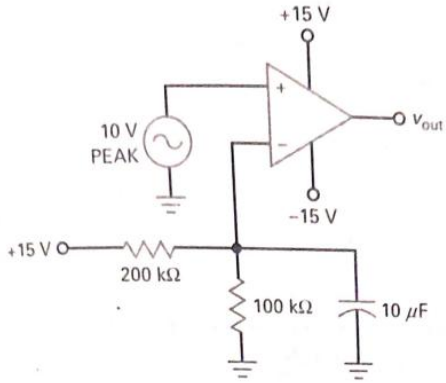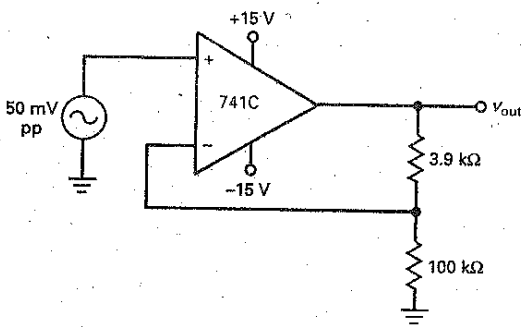	gate voltage		
	b. With neat circuit diagram, develop an expression for voltage gain, input impedance and output impedance for common gate amplifier.	10	L3
OR			
4	a. Develop an expression for drain to source voltage for a MOSFET amplifier using drain to gate feedback resistor.	10	L3
	b. Develop an expression for transconductance in terms of drain current and overdrive voltage.	4	L3
	c. With neat circuit diagram, develop an expression for voltage gain, input impedance and output impedance for common source amplifier without source resistance.	6	L3
MODULE-3			
5	a. With neat circuit diagram, explain the operation of R-2R DAC	7	L2
	b. For the circuit shown in Fig 5b, the input voltage is a sine wave with peak value of 10V. Determine the trip point. Also plot the input output waveform	7	L3
 <p style="text-align: right;">Fig 5b</p>			
	c. With neat circuit diagram, explain the operation of Schmitt trigger.	6	L2
OR			
6	a. With neat circuit diagram, internal diagram of 555 timer and waveforms explain the operation of astable multivibrator.	10	L3
	b. With neat circuit diagram, explain the operation of wein bridge oscillator	10	L3
MODULE-4			
7	a. Classify negative feedback amplifiers and explain each with neat block diagram.	10	L3
	b. Calculate the feedback fraction, ideal closed loop gain, percentage error and exact closed loop voltage gain. Use AOL = 100,000 for 741C	5	L3
			
	c. With neat circuit diagram and expressions, explain current amplifiers.	5	L3
OR			
8	a. Classify the filters and explain the ideal response for each of the	10	L3

	filters.		
	b. With neat circuit diagrams, explain the operation of first order low pass filter and high pass filter	10	L3
MODULE-5			
9	a. With neat circuit diagram and waveform explain SCR phase control using RC circuit	10	L3
	b. With neat circuit diagram, explain the operation of UJT and hence explain how it is used as relaxation oscillator.	10	L3
OR			
10	Make use of break over characteristics to explain the operation of 4 layer diode	10	L3
	Write short notes on IGBT	5	L3
	Explain bi-directional thyristors in brief.	5	L3